

Boolean Algebra & Logic Gates

- A logic is an electronic circuit which
 - operates on binary algebra
 - performs arithmetic and logic functions
 - allows flow of electrons only in one direction
 - alternates between 0 and 1 values
- Positive logic in a logic circuit is one in which
 - logic 0 and 1 are represented by 0 and positive voltage respectively
 - logic 0 and 1 are represented by the negative and positive voltages respectively
 - logic 0 voltage level is higher than logic 1 voltage level
 - logic 0 voltage level is lower than logic 1 voltage level


[U.P.S.C. I.E.S. E.E.-II, 1992]
- The logic is said to be positive if
 - upper level is 0, lower is 1
 - lower level is 0, upper is 1
 - two levels overlap
 - both a) and b) are true
- The voltage levels of a negative logic system
 - must necessarily be negative
 - may be negative or positive
 - must necessarily be positive
 - must necessarily be 0 V and -5 V


[U.P.S.C. I.E.S. E.E.-II, 1999]
- If L = low, H = high, a positive logic is
 - L = 5V, H = 0V
 - L = 5V, H = -5 V
 - L = 5V, H = 1V
 - L = -5V, H = -1V
- Three Boolean operators are:
 - NOT, OR, AND
 - NOT, NAND, OR
 - NOR, OR, NOT
 - NOR, NAND, NOT

[U.P.T.U. Elec. Engg. Even Semester, 2009-10]
- The only function of a NOT gate is to
 - invert an input signal
 - act as a universal gate
 - stop a signal
 - none of the above
- When an input electrical signal A = 101010 is applied to a NOT gate, the output signal will be
 - 111010
 - 101010

- 010101
 - 101011
- A three-input OR gate has output equal to 0 when
 - all its inputs are high
 - two of its inputs are high
 - all are low
 - one is high and the other two are low
 - The output of a 2-input OR gate is zero only when its
 - either inputs is 0
 - either input is 1
 - both inputs are 1
 - both inputs are 0
 - Indicate which of the following logic gates can be used to realize all possible combinational logic functions:
 - OR gates only
 - NAND gates only
 - EX-OR gates only
 - NOR gates only
 - Both b) or d)

[GATE E.C.E.- 1989]
 - The complete set of only those Logic Gates designated as Universal Gates is
 - NOT, OR and AND Gates
 - XNOR, NOR and NAND Gates
 - NOR, and NAND Gates
 - XOR, NOR and NAND Gates

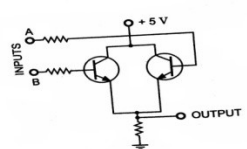[GATE E.E.- 2009]
 - The circuit shown in the given figure is
 - an AND gate
 - an OR gate
 - a XOR gate
 - a NAND gate

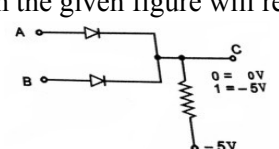[U.P.S.C. I.E.S. E.E.-II, 2000]
 - If negative logic is used, the diode gate shown in the given figure will represent
 - OR gate
 - AND gate
 - NOR gate
 - NAND gate

[U.P.S.C. I.E.S. E.E.-II, 1996]
 - The output Y of the circuit shown in figure is

ENGINEERING ACADEMY DEHRADUN


www.engineeringacademy.co.in

MOB: 08449597123, 09411340612 Prep By: R.K.Raman



- a) $\bar{A}A$ b) A c) 1 d) \bar{A}

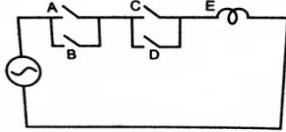16. The switching circuit given in the figure can be expressed in binary logic notation as



- a) $L = (A + B)(C + D)E$
 b) $L = AB + CD + E$
 c) $L = E + (A + B)(C + D)$
 d) $L = (AB + CD)E$

[U.P.S.C. I.E.S. E.E.-II, 1995]

17. An AND gate

- a) implements logic addition
 b) gives high output only when all inputs are low
 c) is equivalent to a series switching circuit
 d) is equivalent to a parallel switching circuit

18. NAND operation with x and y inputs is

- a) $\overline{x+y}$ b) $\bar{x} + \bar{y}$
 c) $\bar{x} \times \bar{y}$ d) $(\bar{x} + \bar{y})(x + y)$

19. The output Y of a NOR gate for inputs A and B is

- a) $\overline{A+B}$ b) $\overline{A+B}$
 c) $\overline{A+B}$ d) \overline{AB}

20. The output of an EX-OR gate with A and B as inputs will be

- a) $AB + \overline{AB}$ b) $(A+B)(\overline{A+B})$
 c) $(A+B)(\overline{AB})$ d) $\overline{A+B} + AB$

[U.P.S.C. I.E.S. E.E.-II, 1998]

21. In exclusive OR gate, when output is zero the inputs are

- a) 0,1 b) 1,0 c) 1,1 d) 1,x

22. An XOR gate can be converted into an inverter by

- a) permanently connecting one input to 1
 b) permanently connecting both inputs to 1
 c) permanently connecting one inputs to 0
 d) permanently connecting both inputs to 0

23. The output of a logic gate is '1' when all its inputs are at logic '0'. Then the gate is either

- a) a NAND or an EX-OR gate
 b) a NOR or an EX-NOR gate
 c) an OR or an EX-NOR gate
 d) an AND or an EX-OR gate

[U.P.S.C. I.E.S. E.T.E.-II, 2003]

24. The idempotent law of Boolean algebra says that

- a) $x + y = 1$ b) $x + x = x$
 c) $x + xy = x$ d) $x(x + y) = x$

25. According to Boolean algebra, which one of the following is incorrect?

- a) $A + 1 = 1$ b) $A + 0 = A$
 c) $A + \bar{A} = 0$ d) $A + A = A$

26. Which one of the following Boolean algebra rule is correct?

- a) $A \cdot \bar{A} = 1$ b) $A + AB = A + B$
 c) $A \cdot \bar{A} \cdot B = A + B$ d) $A(A + B) = B$
 e) $A + A \cdot B$

27. is equal to

- a) $A + B$ b) $\bar{A} + \bar{B}$
 c) A d) $A + 1$
 e) $A \cdot (A + B) =$

28.

- a) B b) A
 c) \bar{A} d) None of these

ENGINEERING ACADEMY DEHRADUN

www.engineeringacademy.co.in

MOB: 08449597123, 09411340612 Prep By: R.K.Raman

29. The logical expression $y = A + \bar{A}B$ is equivalent to
- a) $y = AB$ b) $y = \bar{A}B$
c) $y = \bar{A} + B$ d) $y = A + B$
[GATE E.CE.-II, 1999]
30. The variable A can be written as
- a) $(A + \bar{B}B)$ b) $(B + A)(B + \bar{A})$
c) $(AB + \bar{A}\bar{B})$ d) $(B + A\bar{A})$
31. The simplified logic expression for $y = \bar{A}B + A\bar{B} + AB$ is
- a) AB b) $\overline{A+B}$
c) $A+B$ d) $\overline{A+B}$
32. The simplified Boolean equation for $F = B[(A + \bar{B})(B + C)]$ is
- a) $AB(1 + C)$ b) $AC(1 + B)$
c) AB d) 0
33. The simplified form of the Boolean expression $\bar{A} + A\bar{B}$ is
- a) $A + B$ b) $A + \bar{B}$
c) $\bar{B} + A$ d) $\bar{A} + \bar{B}$
34. What is the Boolean expression equivalent to? $A \oplus B$
- a) $AB + \bar{A}\bar{B}$ b) $\bar{A}B + A\bar{B}$
35. If A and B are Boolean variables, then what is $(A + B) \cdot (A + \bar{B})$ equal to?
- a) B b) A
c) $A + B$ d) AB
[U.P.S.C. I.E.S. E.T.E -II, 2006]
36. Which of the following Boolean algebra rules is correct?
- a) $A \cdot \bar{A} = 1$ b) $A + AB = A + B$
c) $A + \bar{A}B = A + B$ d) $A(A + B) = B$
[U.P.S.C. I.E.S. E.T.E -II, 2009]
37. The Boolean expression $Y = AB + (A + B)(\bar{A} + B)$ may be simplified as
- a) $Y = A$ b) $Y = \bar{A}$
c) $Y = B$ d) $Y = \bar{B}$
[U.P. Technical Univ. 2008-9]
38. Which one of the following statements is not correct?
- a) $X + \bar{X}Y = X$ b) $X(\bar{X} + Y) = XY$
c) $XY + X\bar{Y} = X$
d) $ZX + Z\bar{X}Y = ZX + ZY$
[U.P.S.C. I.E.S. E.T.E. II, 2008]
39. d' Morgan law is $\overline{ABC} = \bar{A}\bar{B}\bar{C}$
- a) $\overline{ABC} = \bar{A} + \bar{B} + \bar{C}$
b) $\overline{A+B} = \bar{A} + \bar{B}$
c)

ENGINEERING ACADEMY DEHRADUN

www.engineeringacademy.co.in

MOB: 08449597123, 09411340612 Prep By: R.K.Raman

40. $\overline{A+B+C} = \bar{A} + \bar{B} + \bar{C}$, when demorganised, give
- a) $A \cdot \bar{B} + C \cdot \bar{D}$ b) $A \cdot \bar{B} + \bar{C} \cdot D$
 c) $\bar{A} \cdot B + \bar{C} \cdot D$ d) $\bar{A} \cdot B + C \cdot \bar{D}$
41. The Boolean expression $\overline{A+B+C} + \overline{\bar{A} + \bar{B} + \bar{C}} + \overline{A+B+C} + ABC$ are reduces to
- a) A b) B c) C
 d) $A+B+C$
- [U.P.S.C. I.E.S. E.T.E. II, 2010]
42. $\overline{A+BC}$ is
- a) $A+B+C$ b) ABC
 c) $A+\bar{B}\bar{C}$ d) $(A \cdot \bar{B} + \bar{C})$
 $f = x \cdot y + \bar{x} \cdot \bar{y}$
43. The logic function is the same as
- a) $f = (x+y)(\bar{x} + \bar{y})$
 b) $f = (\bar{x} + \bar{y})(x+y)$
 c) $f = (\bar{x} \cdot \bar{y})(x \cdot y)$
 d) None of these
- [U.P.S.C. I.E.S. E.T.E -II, 2011]
44. Use of De Morgan's theorem on $Z = \overline{AC(ABD)}$
- a) $\bar{A}\bar{C}(A+\bar{B}+\bar{D})$ b) $AC(A+\bar{B}+\bar{D})$
- c) $\bar{A}\bar{C}(A+\bar{B}+\bar{D})$ d) $\bar{A}\bar{C}(\bar{A}+B+D)$
45. The expression $(X+Y)(X+\bar{Y})(\bar{X}+Y)$ is equivalent to
- a) $\bar{X}\bar{Y}$ b) $\bar{X}Y$
 c) $X\bar{Y}$ d) XY
- [U.P.S.C. I.E.S. E.E -II, 1998]
46. The Boolean expression $X = B + A \cdot \bar{B} + A \cdot B$ is equivalent to
- a) $A+B$ b) $\bar{A} \cdot B$
 c) $\overline{A+B}$ d) $A \cdot B$
- [U.P.S.C. I.E.S. E.E -II, 2005]
47. The Boolean expression $\overline{YZ + XZ + XY}$ is logically equivalent to
- a) $YZ + \bar{X}$ b) $YZX + \bar{X}\bar{Y}\bar{Z}$
 c) $YZ + XZ + XY$
 d) $\overline{XYZ} + \overline{X\bar{Y}\bar{Z}} + \overline{X\bar{Y}Z} + \overline{X\bar{Y}\bar{Z}}$
- [U.P.S.C. I.E.S. E.E -II, 2005]
48. The Boolean expression $ABCD + \bar{A}\bar{B}\bar{C}\bar{D} + ABC\bar{D} + \bar{A}\bar{B}C\bar{D}$ is equivalent to
- a) A b) AC c) ABC d) 1
- [U.P.S.C. I.E.S. E.E -II, 2008]
49. $\overline{ABC} + \overline{ABC} + \overline{ABC} + \overline{ABC}$ is equal to
- a) A b) B
 c) C d) None of these
50. The simplified form of the Boolean expression $Y = (\bar{A} \cdot BC + D)(\bar{A} \cdot D + \bar{B} \cdot \bar{C})$

ENGINEERING ACADEMY DEHRADUN

www.engineeringacademy.co.in

MOB: 08449597123, 09411340612 Prep By: R.K.Raman

can be written as

$$\bar{A} \cdot D + \bar{B} \cdot \bar{C} \cdot D$$

a)

$$AD + B \cdot \bar{C} \cdot D$$

b)

$$(\bar{A} + D)(\bar{B} \cdot C + \bar{D})$$

c)

$$A \cdot \bar{D} + B \cdot C \cdot \bar{D}$$

d)

[GATE E.E., 2004]

$$F = (A + B)(A + C)$$

51. In Boolean algebra, if then

$$F = AB + \bar{A}C$$

a)

$$F = AC + \bar{A}B$$

c)

$$F = AB + \bar{A}\bar{B}$$

b)

$$F = \bar{A}\bar{A} + \bar{A}B$$

d)

[U.P.S.C. I.E.S. E.E -II, 2001]

52. The simplified form of a logic function

$$Y = \overline{(\bar{A}B)} \cdot \overline{(\bar{A}B)}$$

is

$$A + B$$

a)

$$\bar{A} + \bar{B}$$

c)

$$AB$$

b)

$$\bar{A}B + \bar{A}\bar{B}$$

d)

[U.P.S.C. I.E.S. E.E -II, 2003]

53. Which one of the following is equivalent to the Boolean expression

$$Y = \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{C}\bar{A} = ?$$

$$\overline{AB + BC + CA}$$

a)

$$(\bar{A} + \bar{B})(\bar{B} + \bar{C})(\bar{A} + \bar{C})$$

b)

$$(A + B)(B + C)(C + A)$$

c)

$$\overline{(A + B)(B + C)(C + A)}$$

d)

[U.P.S.C. I.E.S. E.E -II, 2001]

54. The AND function can be realized by using only n number of NOR gates. What is n equal to?

a) 2

b) 3

c) 4

d) 5

[U.P.S.C. I.E.S. E.E -II, 2008]

Boolean Algebraic Logic

Gates Answers Key

1. b	51. c
2. d	52. d
3. b	53. c
4. b	54. b
5. d	
6. a	
7. a	
8. c	
9. c	
10. d	
11. e	
12. c	
13. b	
14. a	
15. d	
16. a	
17. c	
18. b	
19. b	
20. c	
21. c	
22. a	
23. b	
24. b	
25. c	
26. c	
27. c	
28. b	
29. d	
30. a	
31. c	
32. c	
33. d	
34. b	
35. b	
36. c	
37. c	
38. a	
39. b	
40. c	
41. b	

ENGINEERING ACADEMY DEHRADUN

www.engineeringacademy.co.in

MOB: 08449597123, 09411340612 Prep By: R.K.Raman

42. b	
43. b	
44. a	
45. d	
46. a	
47. d	

48. b	
49. c	
50. a	

