

1. The condition for the validity of ohm's law is that the
- Temperature should remains constant
  - Current should be proportional to voltage
  - Resistance must be wire wound type
  - All of the above
- Ans-d
2. Twelve  $1\ \Omega$  resistances are used as edges to form a cube. The resistance between two diagonally opposite corners of the cube is
- $5/6\ \Omega$
  - $1\ \Omega$
  - $6/5\ \Omega$
  - $3/2\ \Omega$
- Ans-a
3. Ideal voltage source have
- Zero internal resistance
  - Infinite internal resistance
  - Low value of current
  - Large value of emf.
- Ans-a
4. Ideal current source have
- Zero internal resistance
  - Infinite internal resistance
  - Low value of voltage
  - Large value of current
- Ans-b
5. For a network of 11 branches and 6 nodes, what is the number of independent loops
- 4
  - 5
  - 6
  - 11
- Ans-c
6. If an atom loses one or more electrons it becomes
- electrically neutral
  - electrically positive
  - electrically
  - a neutral ion
- ans-b
7. The space surrounding a charge body, within which the influence of its charge extends is called
- coulombs
  - electric field
  - electric intensity
  - lines of force
- ans-b
8. The unit of electric energy is
- Watt
  - joule-second
  - KWh
  - Volt-Ampere
- Ans-c
9. Permittivity is expressed in terms of
- N/m
  - Webers/m

- (c) Farad/meter  
(d) Farad/sq.m.

Ans-c

10. The S.I. unit of power is

- (a) Henry (b) coulomb  
(c) watt (d) watt-hour

Ans-c

11. The substances which have a large number of free electrons and offer a low resistance are called

- (a) insulators (b) inductors  
(c) semi-conductors (d) conductors

Ans-d

12. Electric current passing through the coil produces

- (a) magnetic effect  
(b) luminous effect  
(c) thermal effect  
(d) chemical effect

Ans-a

13. Bulbs in street lighting are all connected in

- (a) parallel (b) series  
(c) series-parallel (d) end-to-end

Ans-a

14. Temperature co-efficient of resistance is expressed in terms of

- (a) ohms/°C  
(b) mho/ohm °C  
(c) /°C  
(d) mhos/°C

Ans-c

15. The resistance of a conductor varies inversely as

- (a) length

- (b) area of cross-section  
(c) temperature  
(d) resistivity

Ans-b

16. Which of the following materials has a negative temperature coefficient of resistance?

- (a) Copper (b) Aluminum  
(c) Carbon (d) Brass

Ans-c

17. Which is the best conductor of electricity?

- (a) Iron (b) Silver  
(c) Copper (d) Carbon

Ans-b

18. The rating of a fuse wire is always expressed in

- (a) ampere-hours (b) ampere-volts  
(c) kWh (d) amperes

Ans-d

19. A closed switch has a resistance of

- (a) zero  
(b) about 50 ohms  
(c) about 500 ohms  
(d) infinity

Ans-a

20. The ratio of mass of proton to that of electron is nearly

- (a) 1840 (b)  $\frac{1}{1840}$   
(c) 30 (d) 4

Ans-a

21. What will be the capacity of four capacitors of equal capacity 'C', when connected in series

- (a) 4C                      (b) C/4  
(c) C                        (d) 3/4C

Ans-b

22. A bank of condenser across the load of the factory is used.

- (a) for improving the power factor  
(b) for reducing the power factor  
(c) for improving the fluctuations  
(d) for quick starting of the motors

ans-a

23. The electric flux and field intensity inside a conducting sphere is

- (a) zero                      (b) maximum  
(c) uniform                (d) minimum

Ans-a

24. Dielectric strength of air is nearly

- (a) 30 kV/cm (max)  
(b) 30 kV/mm  
(c) 300 kV/mm  
(d) 3000kV/mm

Ans-a

25. The potential inside a charged hollow sphere is

- (a) zero  
(b) same as that on the surface  
(c) less than that on the surface  
(d) None of these

Ans-b

26. The capacity of capacitor used in power factor correction is expressed in terms of

- (a) kVA                      (b) kW  
(c) volts                    (d) kVAR

Ans-d

27. Which of the following expression is correct for electric field strength ?

- (a)  $E = D/\epsilon$   
(b)  $E = D^2/t$   
(c)  $E = jtD$   
(d)  $E = nD^2$

Ans-a

28. The absolute permittivity of free space is given by

- (a)  $8.857 \times 10^{-9}$  F/m  
(b)  $8.857 \times 10^{-10}$  F/m  
(c)  $8.857 \times 10^{-11}$  F/m  
(d)  $8.854 \times 10^{-12}$  F/m

Ans-d

29. The relative permittivity has the following units

- (a) F/m  
(b) m/F  
(c) Wb/m  
(d) no units

ans-d

30. The unit of electric field intensity is

- (a) N/C<sup>2</sup>  
(b) Wb/m<sup>2</sup>  
(c) N/C

(d)  $N^2/C$ 

Ans-c

31. One kilo-watt-hour is equal to

- (a) 4180 kilo calories
- (b) 829 kilo calories
- (c) 860 kilo calories
- (d) 4200 kilo calories

Ans-c

32. The direction of the induced current depends upon.

- (a) the length of the conductor
- (b) the speed of the movement of the conductor
- (c) the strength of the magnetic field
- (d) the direction of the magnetic field

ans-d

33. The sign  $\otimes$  in a plan view of a conductor means

- (a) the current flows into the drawing area
- (b) the current flows out of the drawing area
- (c) there is a positive current in the conductor
- (d) we cannot apply the cork screw rule

ans-a

34. The aim of shielding an instrument is

(a) to prevent its damage due to moisture

- (b) to reduce the effect of stray magnetic fields on its reading
- (c) to increase the range of the instruments
- (d) none of these

ans-b

35. The magnitude of e.m.f. induced in a wire does not depend on

- (a) length of wire
- (b) speed of wire
- (c) diameter of wire
- (d) none of these

ans-c

36. An e.m.f. of 8 V is induced in a coil of inductance 4H. The rate of change of current must be

- (a) 32 A/s
- (b) 0.5 A/s
- (c) 2A/sec
- (d) None of these

Ans-c

37. Air gap has \_\_\_\_\_ reluctance as compared to iron or steel path

- (a) little
- (b) lower
- (c) higher
- (d) zero

Ans-c

38. The unit of relative permeability is

- (a) henry/metre
- (b) henry
- (c) henry/sq. m
- (d) it is dimensionless

Ans-d

39. One Telsa is equal to

- (a)  $1 \text{ Wb/mm}^2$
- (b)  $1 \text{ Wb/m}$
- (c)  $1 \text{ Wb/m}^2$
- (d)  $1 \text{ mWb/m}^2$

Ans-c

40. Permeability in a magnetic circuit corresponds to \_\_\_\_\_ in an electric circuit.

- (a) resistance
- (b) resistivity
- (c) conductivity
- (d) conductance

Ans-c

41. The unit of retentivity is

- (a) Weber
- (b) Weber/sq. m
- (c) Ampere turn/mete
- (d) Ampere turn

Ans-b

42. The unit of flux is the same as that of

- (a) Reluctance
- (b) Resistance
- (c) Permeance
- (d) pole strength

Ans-d

43. The Biot-savart's law is a general modification of

- (a) Kirchhoffs law
- (b) Lenz's law
- (c) Ampere's law
- (d) Faraday's laws

Ans-c

44. Which form of energy can be easily converted into other forms of energy

- (a) Mechanical Energy
- (b) Electrical Energy
- (c) Chemical Energy
- (d) Heat Energy

Ans-b

45. Charging of battery is done by

- (a) A.C.
- (b) D.C.
- (c) A.C. or D.C.
- (d) None of these

Ans-b

46. A.C.

- (a) Changes it's direction periodically
- (b) Always flows in the same direction
- (c) Changes it's magnitude as well direction periodically
- (d) Has no change in magnitude or direction

Ans-c

47. The value of Power factor when phase difference between voltage and current is  $0^\circ$

- (a) Unity
- (b) Lagging
- (c) Leading
- (d) None of these

Ans-a

48. If the area cross-section area of a conductor is doubled, its resistance (R) becomes

- (a)  $2R$  (b)  $\frac{R}{2}$   
(c)  $\frac{2}{R}$  (d)  $\frac{3}{2}R$

Ans-b

50. If specific resistance of a material is more, its resistance will be

- (a) More  
(b) Average  
(c) Less  
(d) None of these

Ans-a

51. The energy meter measures the energy in

- (a) Watts  
(b) Kilo-watts  
(c) Kilo-Watt-hour  
(d) Mega watts

Ans-c

52. KVA is the unit of

- (a) Actual-Power  
(b) Apparent Power  
(c) Reactive Power  
(d) None of these

Ans-b

53. If 1 A current flows in a wire of  $2.5\Omega$  resistance, the power lost in form of heat is

- (a) 2.5 watts

- (b) 5 watts  
(c) 1 watt  
(d) 0.4 watt

Ans-a

54. The moving part in an energy meter is

- (a) Magnet  
(b) Colls  
(c) Terminals  
(d) Aluminium disc

Ans-d

55. Lights and ceiling fans are controlled by switches of

- (a) 2 A (b) 5 A (c) 15 A  
(d) 25 A

Ans-b

56. The supply to various sub-circuits is given from

- (a) Main switch  
(b) Distribution board  
(c) Service line  
(d) Energy meter

Ans-b

57. A device used for making and breaking the electrical circuit is

- (a) Fuse (b) Plug  
(c) Junction box (d) Switch

Ans-d

58. Which wiring system is most suitable for temporary wiring

(a) Wooden casing and capping wiring

(b) Lead sheathed wiring

(c) Cleat wiring

(d) Conduit wiring

Ans-c

59. Casing and capping wiring is commonly used for

(a) Residential and office buildings

(b) Outdoor wiring

(c) Damp conditions

(d) Sunny conditions

Ans-a

60. Which of following is kept in mind. While making a choice of wiring system for a building

(a) Type of wire

(b) Nature of load

(c) Material Used

(d) All of these

d

61. Industrial wiring requires

(a) 2-phase, 3-wire supply

(b) 3-phase, 3-wire supply

(c) 3-phase, 4-wire supply

(d) None of these

Ans-b

62. A switch is provided on

(a) Phase wire

(b) Neutral wire

(c) Earth wire

(d) None of these wires

Ans-a

63. Five resistances of  $1.0\Omega$  each are available. The minimum resistance by combining all these will be

(a)  $1\Omega$

(b)  $5\Omega$

(c)  $\frac{1}{10}\Omega$

(d)  $\frac{1}{5}\Omega$

Ans-d

64. Three resistance each of  $R\Omega$  are connected to form a triangle. The resistance between any two terminals will be

(a)  $R\Omega$

(b)  $\frac{3}{2}R\Omega$

(c)  $3R\Omega$

(d)  $\frac{2}{3}R\Omega$

Ans-d

65. Three capacitors of values  $2\mu F$ ,  $4\mu F$  and  $4\mu F$  are connected in parallel, the capacitance of the combination is

(a)  $8\mu F$

(b)  $10\mu F$

(c)  $1\mu F$

(d) None of these

Ans-b

66. The phase displacement between various phases of a 3-phase system is equal to,

(a)  $90^\circ$

(b)  $180^\circ$

(c)  $120^\circ$

(d)  $360^\circ$

PRE.BY- R.K. RAMAN

Ans-c

67. In a balanced 3-phase delta connected system, the relationship between the rms values of line currents and the phase current is given by,

(a)  $I_L = I_{ph}$  (b)  $I_L = \sqrt{3}I_{ph}$

(c)  $I_{ph} = \sqrt{3}I_L$  (d)  $I_L = \sqrt{2}I_{ph}$

Ans-b

68. The apparent power and active power drawn are equal for an ac circuit of,

- (a) inductive type
- (b) capacitive type
- (c) resistive type
- (d) none of these

Ans-c

69. Capacitive reactance of the above circuit is expressed as,

(a)  $X_c = \omega c$  (b)  $X_c = \frac{1}{\omega c}$

(c)  $X_c = \frac{\omega}{c}$  (d)  $X_c = \frac{c}{\omega}$

Ans-b

70. The power factor of a purely inductive circuit is,

- (a) lagging (b) leading
- (c) zero lagging (d) unity

Ans-c

71. The power factor of a pure capacitive circuit is always

- (a) lagging (b) leading
- (c) unity (d) zero leading

Ans-d

72. A cycle of ac wave can be represented by,

- (a)  $\pi$  radians (b)  $2\pi$  radians
- (c)  $180^\circ$  (d) none of these

Ans-b

73. The rms value of voltage for ac sine wave in terms of its maximum value,  $E_{\max}$  is,

- (a)  $\frac{E_{\max}}{\pi}$  (b)  $0.637 E_{\max}$
- (c)  $0.707 E_{\max}$  (d)  $0.5 E_{\max}$

Ans-c

74. Two current wave shapes are represented by,  $i_1 = I_{\max 1} \sin(\omega t)$ ;  $i_2 = I_{\max 2} \sin(\omega t + 30^\circ)$ ; . The current wave  $i_1$  is,

- (a) lagging the current  $i_2$  wave by  $30^\circ$
- (b) leading the current  $i_2$  wave by  $30^\circ$
- (c) in phase with current wave  $i_2$
- (d) none of these

ans-a

75. The maximum transmission voltage used in India is:

- (a) 66 KV (b) 132 KV



(c) 220 KV                      (d) 765 KV

Ans-d

76.Which of following is not a component of a transmission line?

(a) Supports                      (b) Generator

(c) Conductor                      (d) Insulator

Ans-b